

## Q2.1

There are a total of 4 inverters and 2 transmission gates in this topology. This circuit is essentially 2 tri-state inverters and 2 inverters.

## Q2.2


Transient Response

Fri May 3 15:17:27 2024 1

Name ... bit

/B<0:7>

/L<0:7>

 


# Transient Response

Fri May 3 15:17:27 2024 1

Name	...	bit
------	-----	-----

/B<0:7>	
/L<0:7>	

 

When  $EN = 0$  and  $EN\_B = 1$ , then  $V_{out}$  returns the previously stored value in the tri-state inverter with a propagation delay. When  $EN = 1$ , and  $EN\_B = 1$ , then  $V_{out}$  returns  $V_{in}$ , and also stores  $V_{in}$  inside of the tri-state diagram for future usage with the same propagation delay.


Q2.3

## Transient Response

Sat May 4 09:49:44 2024 1

Name ... bit

/B<0:7>

 

The counter circuit counts the number of voltages that they receive as inputs, and they count the number of voltages that they receive as logic value '1' and return the total number of logic value '1's total that it has received.

The latch circuit is a circuit meant to store information to be used at a different point, and if there is high impedance in the transmission gate, the stored information

Q2.4

If EN and ENB were to be accidentally swapped, then the transmission gates would be doing the complete opposite effects within the circuit. If the transmission gates were initially supposed to be returning an inverted version of the data, then with the swap, they would now return high impedance, and return the previously stored value within the transmission gates

Q3.1

If V1 is turned on, Vo is  $V/24$

Q3.2

If V2 is turned on,  $V_o$  is  $V/12$

Q3.3

If V3 is turned on,  $V_o$  is  $V/6$

Q3.4

If V4 is turned on,  $V_o$  is  $V/3$

Q3.5

For maximum  $V_o$ , we would turn on V4, which has max  $V_o$  of  $V/3$

Q3.6

For minimum  $V_o$ , we would turn on V1, which has min  $V_o$  of  $V/24$

Q3.7


The smallest change that can be made is from V1 to V2, which has a difference of  $V/12 - V/24$ , which is equal to  $V/24$ . With 4 bits, a total of 16 different voltages can be generated with the 4 bits

Q3.8

# Transient Response

Sat May 4 09:57:43 2024 1

Name	---	bit
/net010	<input checked="" type="checkbox"/>	
/B<1:3>	<input type="checkbox"/>	

 

Q3.9


15k



# Transient Response

Sat May 4 10:33:57 2024 1

Name	bit
/net010	<input checked="" type="checkbox"/>
/B<1:3>	<input type="checkbox"/>

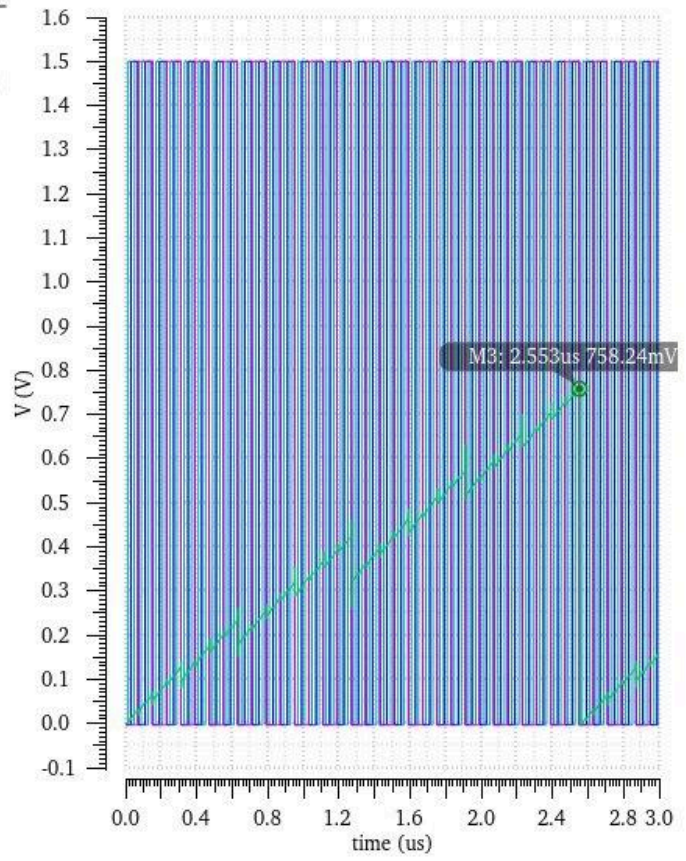

10k


# Transient Response

Sat May 4 10:30:43 2024 1

Name --- bit

/net010


/B<1:3>

 

5k

# Transient Response

Sat May 4 10:16:55 2024 1

 

Q3.10

3R after merging all resistors into 1 for the DAC 8 given R and 2R. This impacts the output range of the DAC, the overall resistance of the DAC remains consistent, which helps reduce potential noise. To bring the data closer to the no load case, we would change the impedance towards the very left of the DAC to bring it closer to the no load case.

Q3.11

If the DAC is wired straight in instead of the latch, then the signal being sent is less stable due to the larger fluctuation in voltage, and the noise can actually end up modifying the initial data being sent, whereas having a latch would allow the data to be loaded safely by saving it. Furthermore, storing data is essential for sequential processing to ensure the safety of each piece of data in the sequence.


Q4.1



We put VSS as negative voltage since the range of output voltage starts to involve negative voltage, so a negative VSS would help keep Vout always at 0 or positive voltage.

Q4.2

15k

 

10k


# Transient Response

Sun May 5 16:09:44  
2024

1

Name

/net010

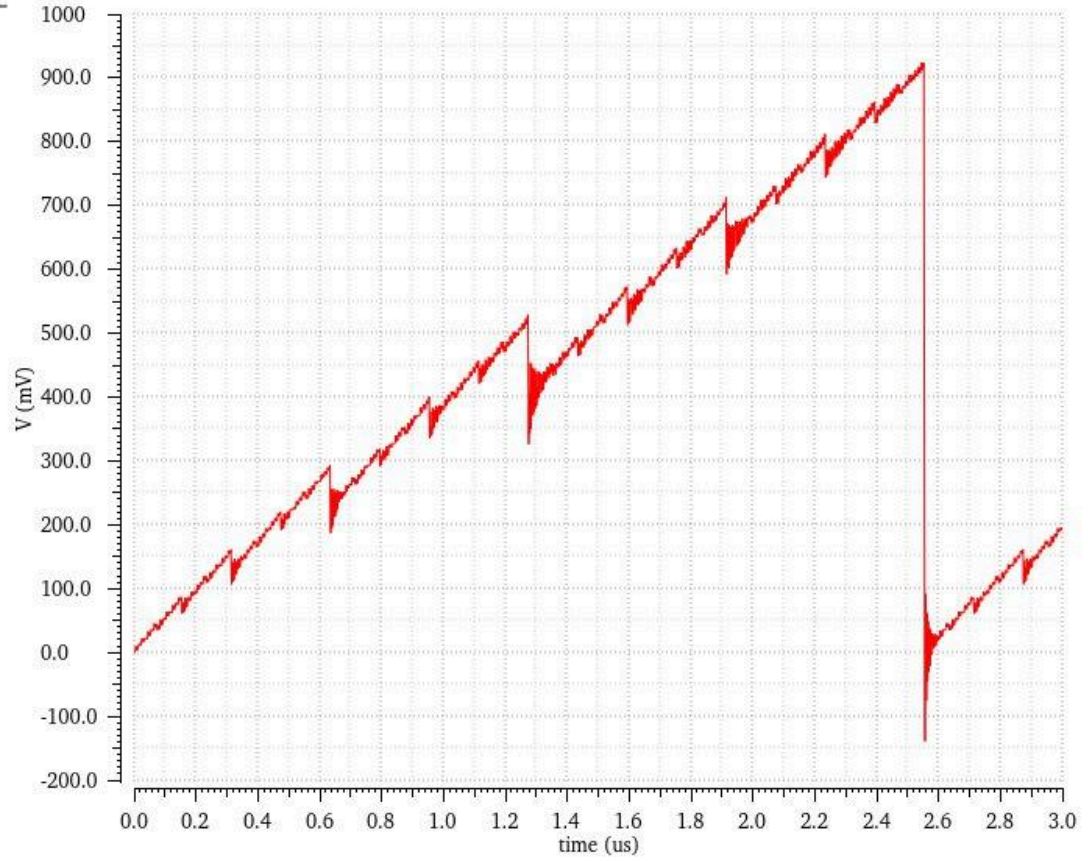

5k


## Transient Response

Sun May 5 16:22:52  
2024

1

Name


/net010

 

The main difference is that the voltage range of Vout conserved for this module at around 950mV, and the signal range gets more vivid, whereas for module 3, as the resistance got lower, so did the Vout voltage.

Q5


Latch DRC

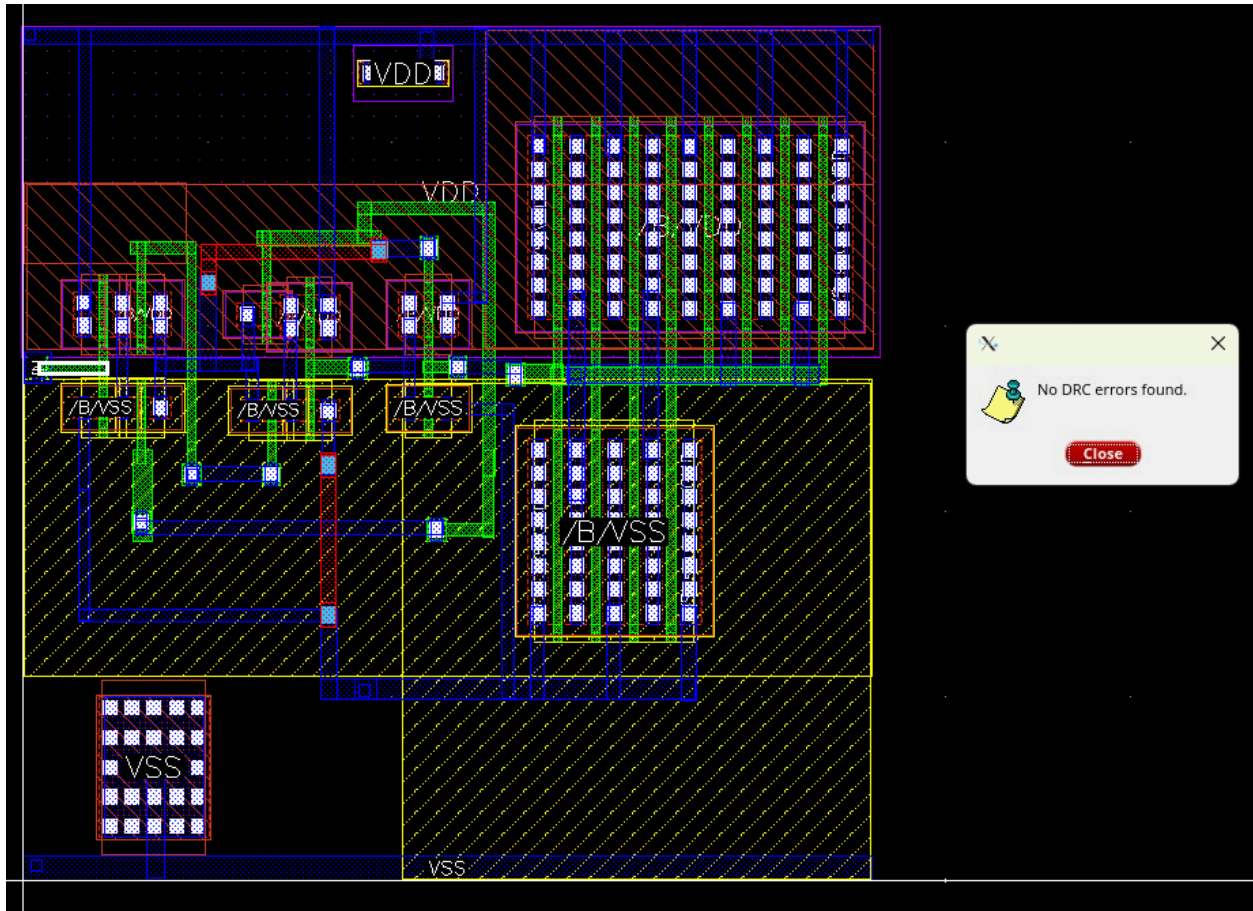

## Latch LVS




DAC DRC

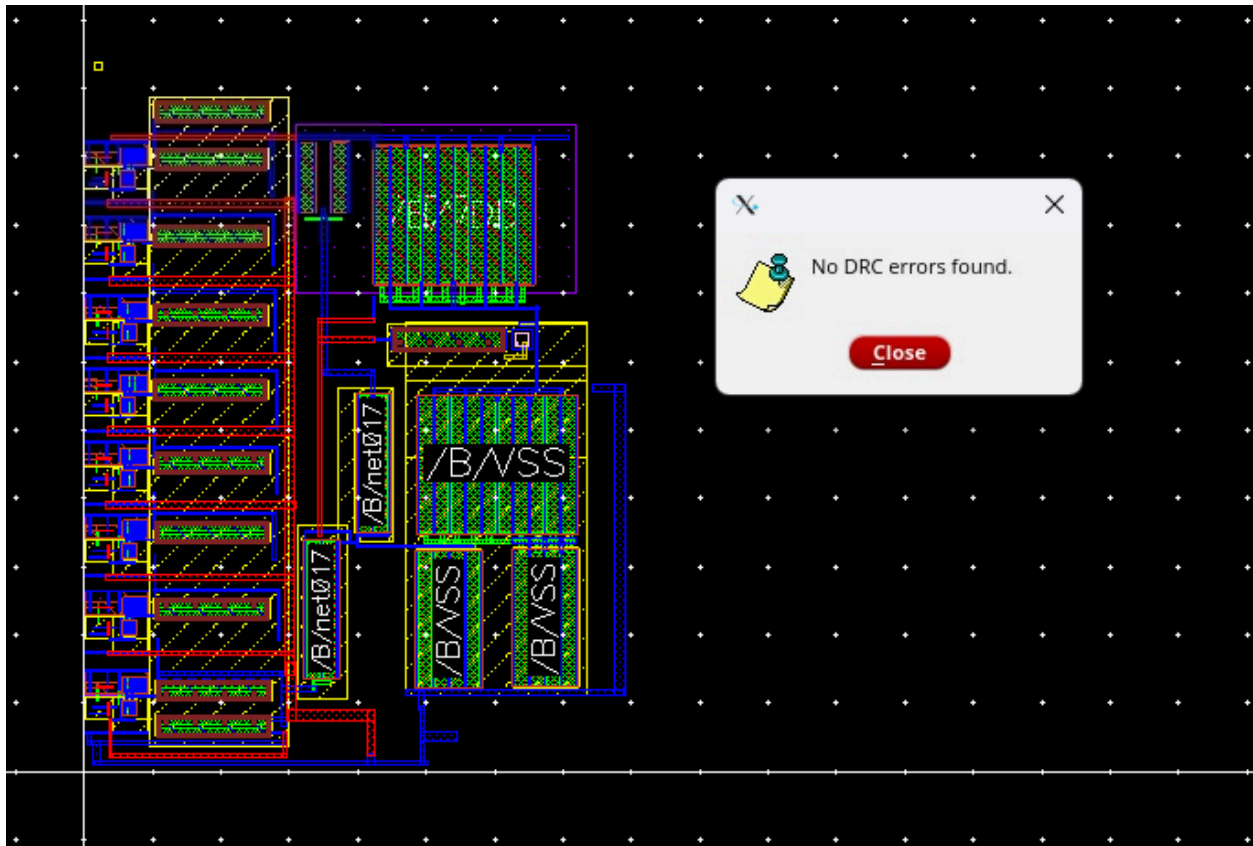

DAC LVS



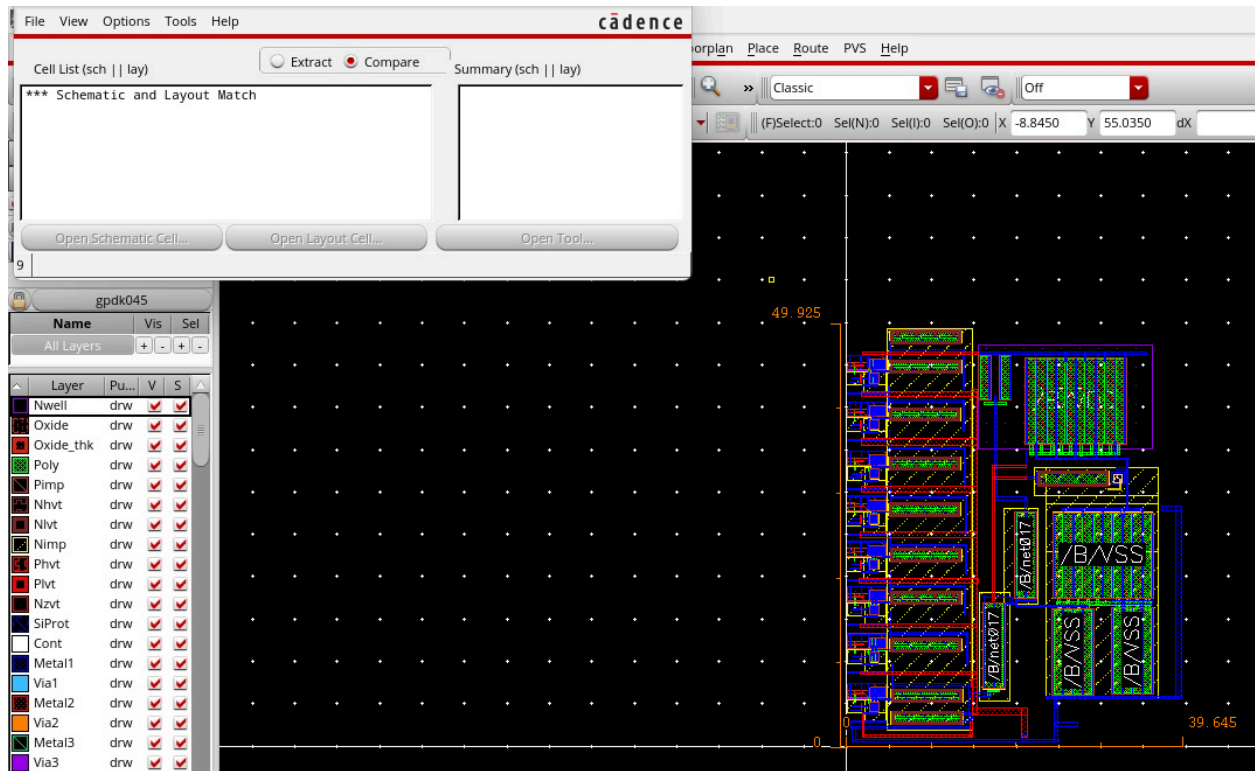

## Reflection:

Throughout the course, we went over several key concepts which laid down the foundation of microcontrollers. We initially went over the concept of NMOS/PMOS fets, and how they can form more complex circuits, as well as potential differences through triode and saturation. To dive deeper into the fundamentals of MOSFETS, we also went over small signal processing, along with more complex circuits involving MOSFETS such as inverters, the involvement of capacitance, and more. Eventually, we wrapped up the semester by going over how MOSFETS could become logic gates such as NAND and NOR, and combining our knowledge to form logic a logic DAC with a latch in the final project.

ECE 18320 1  
MICROELECTC  
CIRCUITS

**MARC DANDIN**

Completed. Thank you!

Survey closes: **May 6 2024 11:59PM**